


$$f = 200 \text{ Hz}$$


$$T = 5 \text{ ms}$$

$$V = 7 \text{ V}$$

$$I_{\text{box}} = 0.2 \text{ V on y-axis}$$
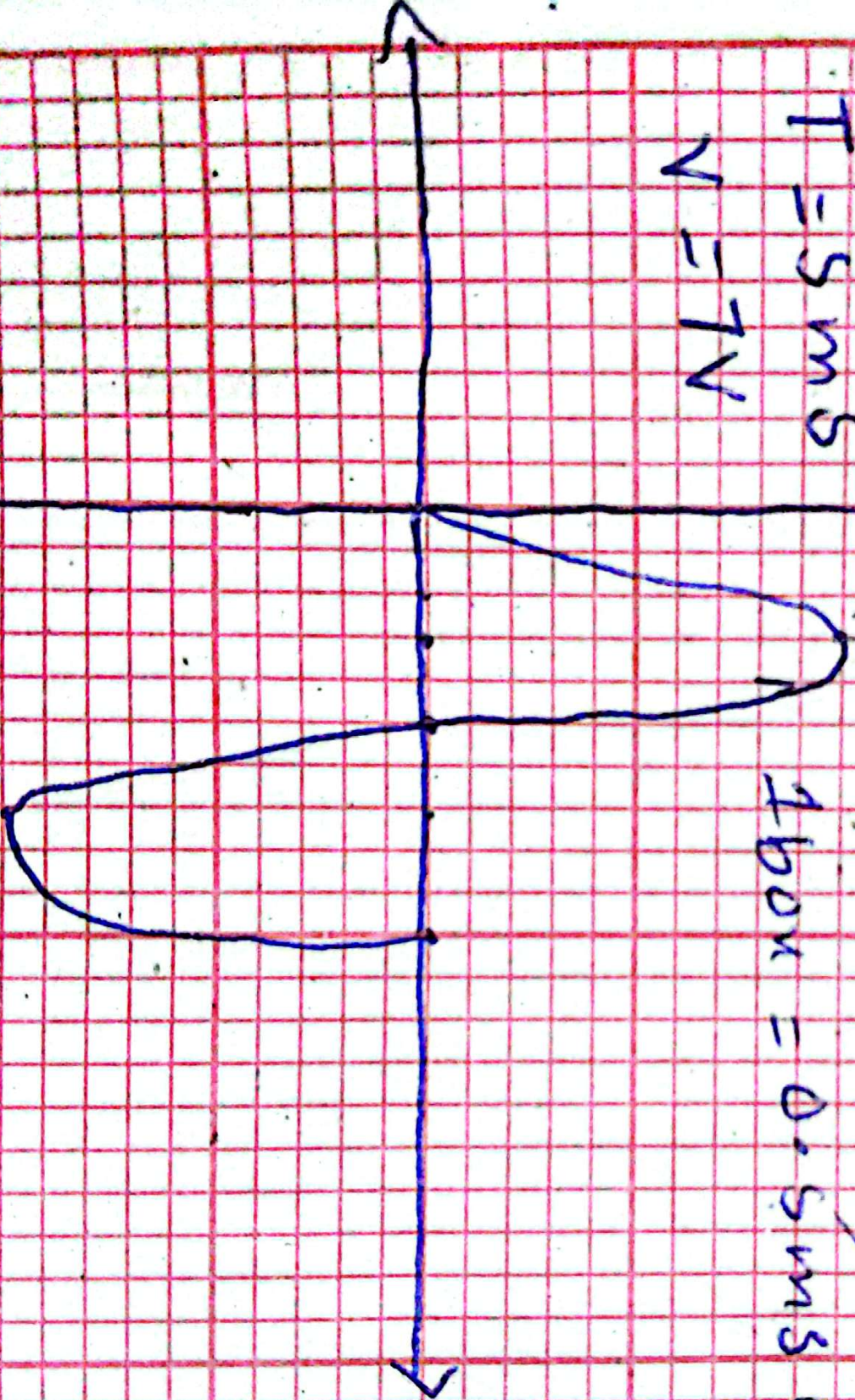
$$I_{\text{box}} = 0.5 \text{ ms on x-axis}$$



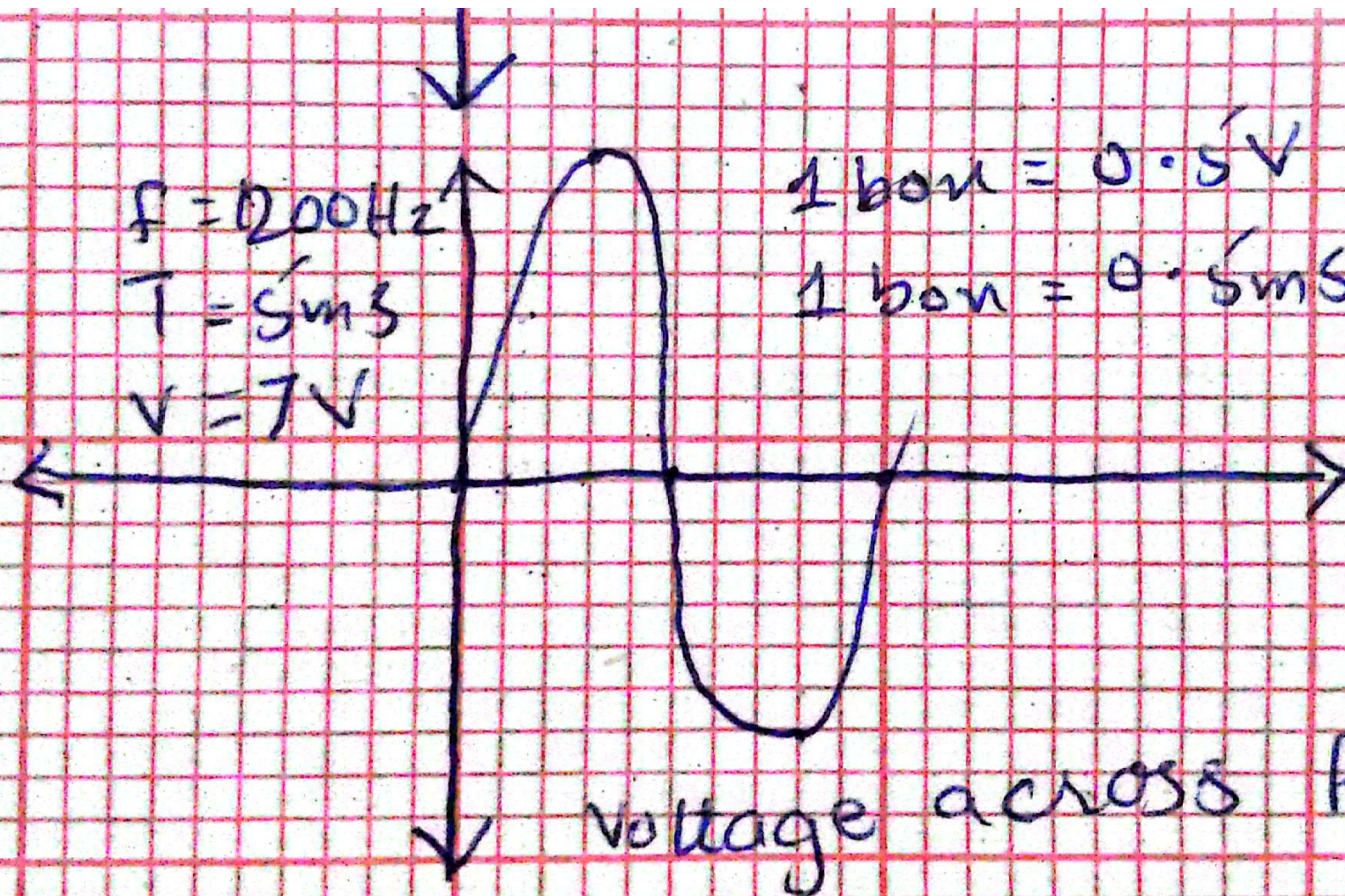


$$f = 200 \text{ Hz}$$

$$T = 5 \text{ ms}$$

$$V = 7 \text{ V}$$

$$1 \text{ box} = 2 \text{ V y-axis}$$
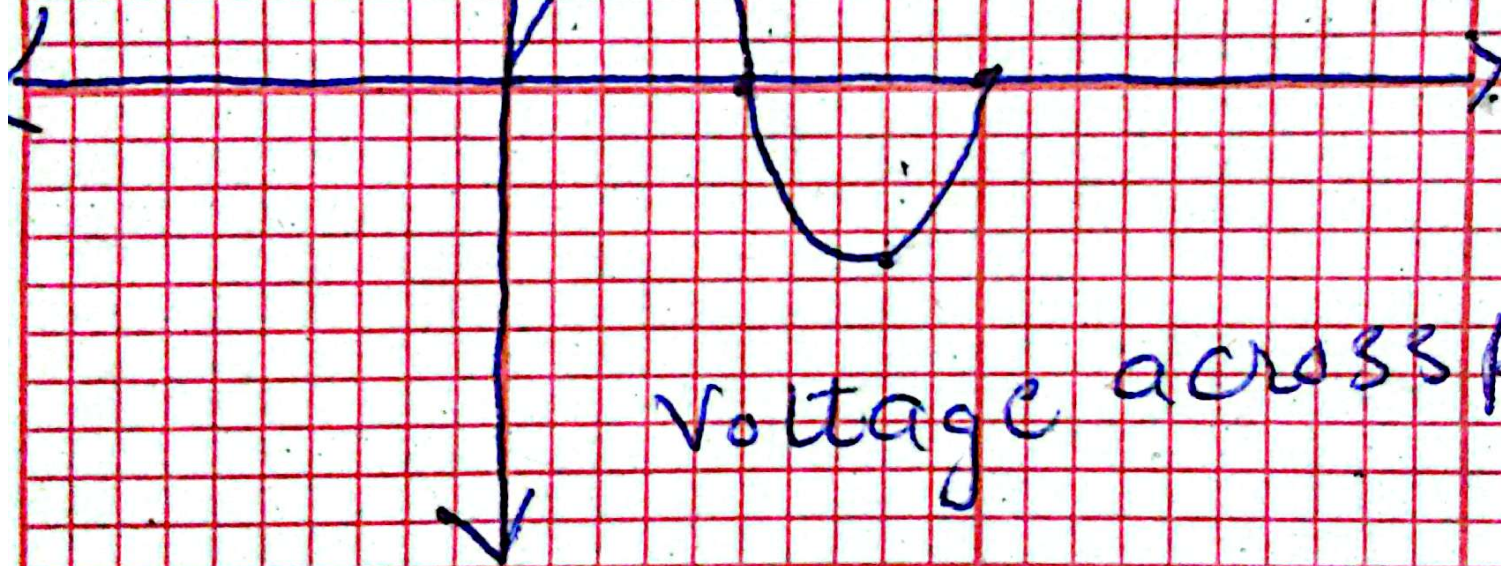
$$1 \text{ box} = 0.5 \text{ ms x-axis}$$



Voltage across R_2


$$f = 200 \text{ Hz}$$

$$T = 5 \text{ ms}$$

$$V = 7 \text{ V}$$

$$1 \text{ box} = 1.5 \text{ V y-axis}$$
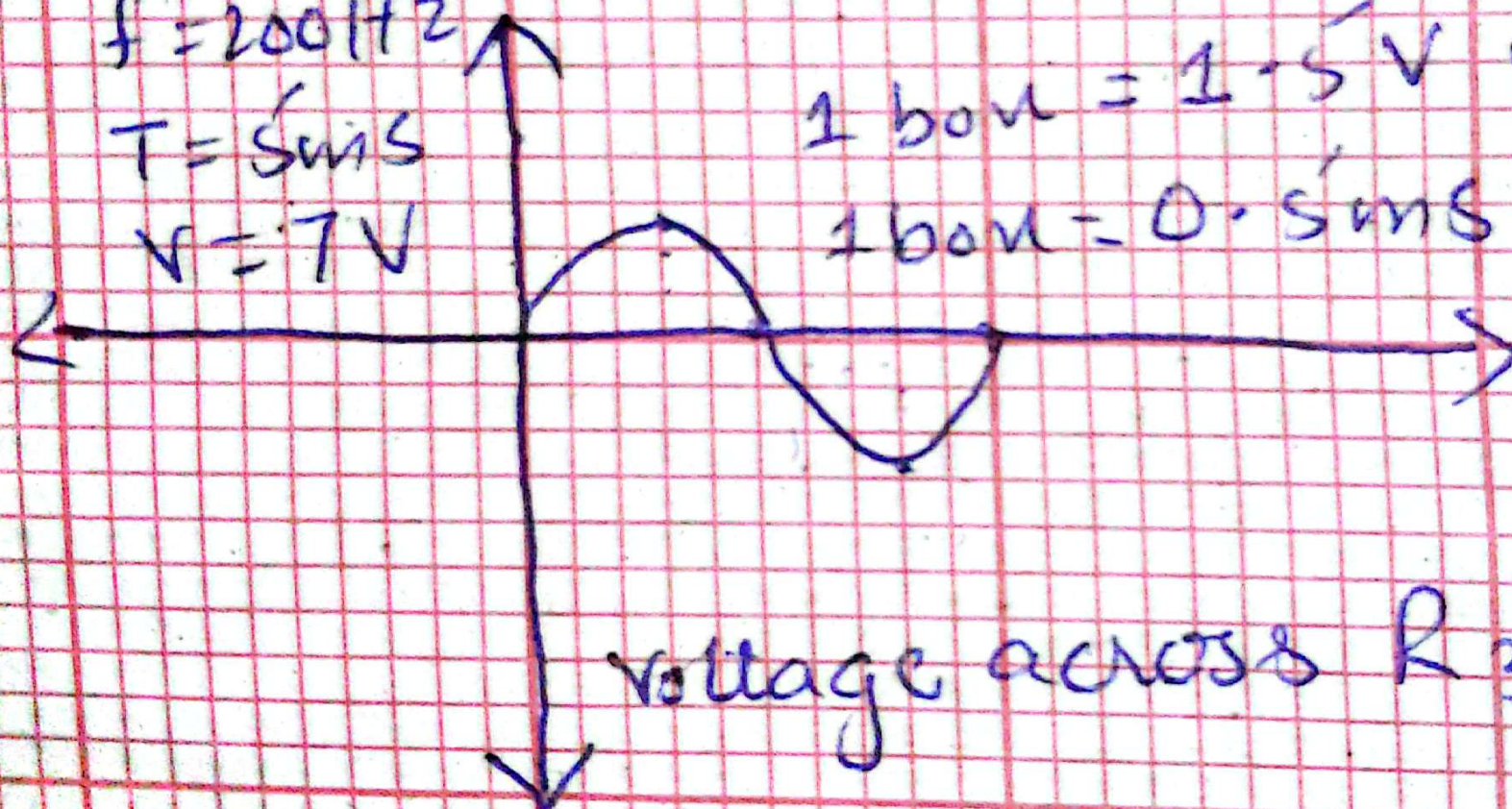
$$1 \text{ box} = 0.5 \text{ ms x-axis}$$



voltage across R_3

